

Hardware Synthesis Using VHDL (Part 1)

VHDL Implementation

Michael presents an XC3S200-based timing system that includes a date/time function, an alarm, and a stopwatch. He used VHDL to get the job done.

Learning something new is never easy. I remember sitting in a brightly lit room surrounded by slackened faces as a presenter droned on and on about VHSIC high-definition language (VHDL). The presenter was an expert in the field who had written a book on the subject. Although he was in demand as a lecturer, his in-depth presentation on VHDL left most of us bored and wondering how to apply what he was teaching.

I'll try to avoid putting you to sleep. My approach is simple: I'll use real-world examples. In this article I'll describe practical aspects of VHDL such as counters, decoders, ROM, state machines, multiplexers, latches, test benches, and much more using a sophisticated stopwatch application (see Figure 1). The application I'll introduce runs on a Xilinx Spartan-3 evaluation board (see Photo 1). Test benches use some constructs that can't be synthesized because they are required to produce a stimulus for testing. I'll warn you about anything that shouldn't be used in a real design. The code constructs are generic VHDL code, which you can use with any synthesis tool. I'll emphasize

VHDL code rather than explain how to use a particular tool because most vendors offer extensive tutorials.

WHAT IS VHDL?

VHDL was developed by the U.S. Department of Defense as a common language for describing hardware designs at the system, component, and gate levels. Its main purpose was to enable the exchange of design data in a common format between different contractors.

VHDL is ideal for producing design descriptions that can be translated or synthesized into real hardware implementations. System-C proponents don't want this known, but VHDL is an excellent system modeling language that can describe hardware components at either a functional or gate level.

WHY VHDL?

VHDL is an IEEE standard (Std-1076) supported by all tool vendors. Professionals use it for describing complex ASICs, producing video-processing FPGAs, generating digital signal-processing applications, and much more. By learning VHDL, you will have

 


Photo 1—Take a look at the Xilinx Spartan-3 starter kit with the watch application running in Stopwatch mode. The seven-segment display is located in the lower right corner. The push buttons on the lower left control the stopwatch. An XC3S200 FPGA positioned above the display runs the watch application.

acquired a skill that's in high demand.

VHDL is extremely readable with a syntactic structure that's similar to Visual Basic and Pascal. It has a powerful, expressive syntax that can define new data types and inherently support team-based programming. One company I know has dozens of VHDL designers working in numerous locations on one design.

Tom Cantrell recently wrote that the future is bright for FPGAs, which will play a large role in mainstream applications ("More Flash, Less Cash," *Circuit Cellar*, 178, May 2005). I agree with Tom, but I'll go further and predict that VHDL will become the premier technology used to define FPGA content either as output from design tools or with direct programming. In combination with VHDL, FPGAs provide a low-cost approach to defining complex hardware designs that were inconceivable only a few decades ago. Perhaps most importantly, using VHDL to define hardware is fun.

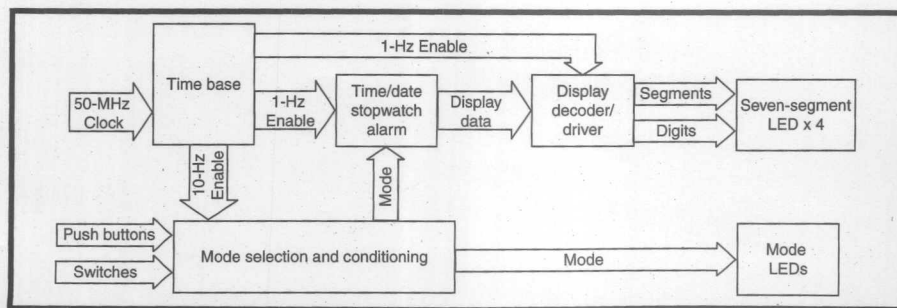


Figure 1—The watch project consists of a time/date function, a second time zone, an alarm, and a stopwatch with lap timing. A time base generates ENABLE signals to run the timing functions, display the multiplexer, and debounce the circuitry.

MY KIND OF TYPE

Data types are to VHDL what colors are to a painter. In this respect, VHDL has almost an infinite palette. Table 1 lists all predefined and standardized (Std-1164) data types along with brief descriptions. The only predefined data type I'll cover in this article is something called a natural number. This type represents an integer with values from zero to the largest representable integer (usually a 32-bit value). Later, I'll define some of my own types when I explain how to implement a state machine.

Although VHDL includes a bit type with values of 0 and 1, this type usually isn't used for synthesis because it doesn't accurately describe the real-world environment. For example, how would you represent a high-impedance state with the bit type?

VHDL Type	Built in	Can be synthesized	Values
std_logic	IEEE	Yes	U, X, 0, 1, Z, W, L, H, -
std_logic_vector	IEEE	Yes	Array (natural range <=>) of std_logic
boolean	Yes	Yes	True or false
integer	Yes	Yes	32 or 64 bits
natural	Yes	Yes	Integers ≥ 0
positive	Yes	Yes	Integers > 0
bit	Yes	Yes	0, 1
bit_vector(natural)	Yes	Yes	Array (natural range <=>) of bits
character	Yes	No	7-bit ASCII
string(positive)	Yes	No	Array (natural range <=>) of characters
text	Yes	No	File of string
time	Yes	No	hr, min, sec, ms, us, ns, ps, fs
delay_length	Yes	No	Time ≥ 0

Table 1—Take a look at some of the data types defined in the Std-1164 and Std-1076 IEEE standards. The most commonly used are the std_logic, std_logic_vector, and natural types.

To address this problem, the IEEE introduced a new type called std_logic, which has values of U (uninitialized), X (unknown), W (weak X), Z (high impedance), H/L (weak 1/0), - (don't care), and, of course, 1 and 0. The power of VHDL allows the definition of a data type to support any user-defined multi-valued logic using enumerations. Of course, to ensure VHDL portability, it's highly

recommended to stick with the std_logic type as defined in the Std-1164 package.

An additional type from the IEEE Std-1164 package is called the std_logic_vector, which consists of a one-dimensional array of std_logic elements. The std_logic_vector is used to represent data buses, addresses, and any other aggregate of bits. Only extremely specific std_logic

values are supported for synthesis purposes: 0, 1, Z, and -. The main reason for this limitation is that the FPGA devices typically contain only gates that respond to 0s and 1s and tristateable buffers using the Z value.

Later, I'll describe how to create a tristate buffer. I'll also explain how the - value is used when simplifying logic. Keep in mind that when creating test benches or device models, all

RabbitCores Do Just About Anything

Theatrical Acrobatics | Rocket Telemetry | Sports Broadcasting | Industrial Automation | Weather & Power Monitoring | Vehicle Tracking | Manufacturing | Security

Packed with features: The reason embedded engineers choose Rabbit Semiconductor for such a wide variety of real-world applications.

RabbitCore Features

- Clock speeds to 51.8 MHz
- Up to 1 MB SRAM / 1 MB Flash
- Up to 54 digital I/O
- Up to 8 analog channels
- Up to 6 serial ports
- Ethernet available with royalty-free TCP/IP stack
- Wireless protocols available
- Complete application and development kits available
- Security and other software modules available
- Complete kits from \$129

Get Your Development Kit Today!


Includes RabbitCore, prototyping board, and complete development software (IDE). For a limited time, get a free copy of *Embedded System Design Using the Rabbit 3000 Microprocessor* with purchase.

www.rabbitcoremodulekits.com

Free Book \$49 Value



RabbitCores From \$22 qty. 1000

 

RABBIT Semiconductor

2932 Spafford Street, Davis, CA 95616
Tel 530.757.8400

9841

of the values of the `std_logic` type can be used to simulate pull-up and pull-down resistors, undefined states, and logic contention.

OPERATORS

VHDL supports several overloaded operators: logical (and, or, nand, nor, xor, and not, which are applicable to Boolean or bit operations); shift (`sll`, `srl`, `sra`, `rll`, and `rsl`, which are only available in some libraries); relational (`=`, `/=`, `<`, `<=`, `>`, and `>=`); arithmetic (`+`, `-`, `*`, `/`, `mod`, `rem`, `**`, and `abs`); and concatenate (&, e.g., two arrays are joined to make a single array).

Any package that introduces a new data type will also overload these operators to enable the manipulation of the new data type and perform conversions to and from existing types and the new data type.

PACKAGES & MORE

I've already cleverly sneaked in the term "package" without really introducing what it means. A package is an encapsulation mechanism used to group related types, constants, and functions or subprograms. Packages are frequently precompiled when the originator prefers not to disclose the source code, but they also can be provided in the form of source code.

The IEEE Std-1164 package is an example of a package supplied with complete source code. I won't describe how packages are created, but I'll refer to functions and types defined in some of the IEEE standard packages. In a real-world project, a package would typically contain the common type and constant declarations and functions required in multiple components. For the purposes of this article, however, the IEEE standard packages will suffice.

Each VHDL component consists of a single entity and one or more architectures. In hardware terms, an entity defines an IC's pins, while the architecture describes the IC's implementation or model. The simplest sort of architecture contains only instantiated components and the wiring interconnects that join the component pins to each other. More complex architectures define detailed functional elements such as counters, registers, state machines, etc.

GETTING STARTED

Listing 1 shows a VHDL implementation of a decade counter somewhat similar to the venerable 74LS90. The first line introduces the standard IEEE library. The next three lines (beginning with `use`) make visible specific packages contained in this standard: `std_logic_1164`, `std_logic_arith`, and `std_logic_unsigned`. The `.ALL` postfix indicates that all of the package's contents are made visible within this context. It's also possible to qualify the export of a specific package declaration using this same dot notation.

COUNTER ENTITY

The counter pins are declared in the entity section of the listing near the top. Five signals are defined: `clk`, `enable`, `reset`, `q`, and `carry`. Like pins on an IC, signals can have three basic modes (or directions): `in`, `out`, or `inout`.

`in` mode signals can be read only. `out` mode signals can be written only. `inout` signals can be read or written. `buffer` mode, a lesser-known mode that can be read or written to, is used primarily for carrying information out of a module. I

don't recommend using `buffer` mode, however, because many synthesis tools have trouble with it.

With the exception of `q`, all other signals are single bits of the `std_logic` type. The `q` signal is your first encounter with a bus or `std_logic_vector`. Typically, bused signal vectors are defined with a bit ordering of `n` down to 0, which means that the leftmost bit `n` is also the most significant bit. The opposite bit ordering (from 0 to `n`) is also possible, but it isn't used too often. The `q` bus has a width of 4 bits.

COUNTER ARCHITECTURE

In the architecture block, the behavioral name distinguishes this architecture from the different implementations. Because my only focus is on producing real hardware, I won't cover multiple architectures.

The `div10_ex` architecture name must be the same name as the entity declaration name and tie this architecture to the entity. The architecture's body is contained in a `begin/end` block with the architecture's name echoed after the end.

Listing 1—This typical VHDL decade counter/divider implementation features an asynchronous reset, a clock enable, and a carry output.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity div10_ex is
    port ( clk : in std_logic;
          enable : in std_logic;
          reset : in std_logic;
          q : out std_logic_vector(3 downto 0);
          carry : out std_logic);
end div10_ex;
architecture Behavioral of div10_ex is
    signal ctr : std_logic_vector(3 downto 0);
begin
    q <= ctr;
    carry <= ctr(3);
    process (clk, reset)
    begin
        if reset = '0' then
            ctr <= (others => '0');
        elsif clk'event and clk = '1' then
            if enable = '1' then
                if ctr = "1001" then
                    ctr <= (others => '0');
                else
                    ctr <= ctr + 1;
                end if;
            end if;
        end if;
    end process;
end Behavioral;
```

Between `is` and `begin` is the declarative region where all constants, types, variables, signals, functions, and component declarations must be made. In this case only a single `ctr` signal is declared with a width of 4 bits. The `ctr` represents the internal decade counter state.

Two signal assignments appear outside the decade counter process just after the `begin` keyword of the architecture. In effect, each of these signal assignments is contained in a process of its own with a sensitivity list con-

taining the signal on the right side of the signal assignment.

In terms of hardware, these signal assignments connect wires between the internal counter state and the external pins identified on the left side of the signal assignment. The reason you can't directly use the signal `q` as the state is because its port is defined as a write-only (or out) port. This is a common occurrence with VHDL out ports. In fact, some people attempt to cheat and define out ports

as being `inout` or `buffer`. Don't do this. Let the data direction be your guide in defining the direction of ports. If the data is truly one-directional, use either the `in` or `out` port. Only bidirectional data flows (e.g., data buses) require `inout` ports.

DECADE COUNTER PROCESS

In the `begin/end` block is a process block. Processes are used to encapsulate a particular behavior of the design (the decade counter behavior in this case). The `clk` and `reset` arguments following the process name form the process's sensitivity list. This process is activated only when signals in the sensitivity list (`clk` or `reset`) change state. Sensitivity lists are used mainly in optimizing simulations so that process activation can be minimized to speed up the simulation. Synthesis tools monitor the sensitivity lists for completeness; they issue warnings if signals are missing, but they don't require them.

If you don't ensure that the sensitivity lists are complete, you may be surprised with some unusual simulation results. You haven't really used VHDL until this sort of simulation bug bites you.

Within a clocked process, you need to include the clock and all other dependent signals outside the clocked region of code in the sensitivity list. The clocked region in this example is demarcated by the `elsif` and `end if` statements.

The asynchronous part of the decade counter is after the first `if` conditional. The `reset = '0'` condition activates the statements following then, which, in this case, clears the `ctr` state.

The `<=` operator is a signal assignment. The signal assignment is different than the variable assignment. Signals are assigned concurrently; variables are assigned sequentially. This may sound like semantics, but it's actually an extremely important point to master. Signal concurrency is a reflection of the fact that all signal transitions in the real world may occur simultaneously. Consequently, all signals within a VHDL project change state simultaneously.

The strange-looking (`others => '0'`) construct is a short-form technique for saying that all the array elements are assigned the 0 value. This

Fighting against your PCB-Design Software?

Here's something that will spare your time and your budget!

Boards designed under EAGLE are found in patient monitoring equipment, chip cards, electric razors, hearing aids, automobiles and industrial controllers. They are as small as a thumbnail or as large as a PC motherboard. They are developed in one-man businesses or in large industrial companies. EAGLE is being used in many of the top companies. The crucial reason for selecting EAGLE is not usually the very favorable price, but rather the ease of use. On top of that comes the outstanding level of support, which at CadSoft is always free of charge, and is available without restriction to every customer. These are the real cost killers!

EAGLE 4.1


Schematic Capture • Board Layout
Autorouter

Now
available
for Mac!

for Windows®
Linux®
Mac®

Version 4.1 Highlights

- ▶ Powerful library management: e.g. move devices between libraries, base library for packages, generate package variants from other libraries.
- ▶ Dynamic ratsnest during routing process.
- ▶ Copy function in schematic.
- ▶ Rotate components in 0.1-degree steps.
- ▶ Blind & buried vias and pads with off-center drill.
- ▶ User-defined background color.
- ▶ Miter function for (rounded) tracks.
- ▶ Smash for groups.
- ▶ Measure distances between arbitrary points.
- ▶ Choose alternative raster on-the-fly with Alt-key.

 

EAGLE 4.1 Light is Freeware!

You can use EAGLE Light for testing and for non-commercial applications without charge. The Freeware Version is restricted to boards up to half Eurocard format, with a maximum of two signal layers and one schematic sheet. All other features correspond to those of the Professional Version. Download it from our Internet Site or order our free CD.

If you decide in favor of the Commercial Light Version, you also get the reference manual and a license for commercial applications. The Standard Version is suitable for boards in Eurocard format with up to 4 signal layers (max. 99 schematic sheets). The Professional Version has no such limitations.

<http://www.CadSoftUSA.com>

800-858-8355

CadSoft Computer, Inc., 801 S. Federal Highway, Delray Beach, FL 33483
Hotline (561) 274-8355, Fax (561) 274-8218, E-Mail: info@cadsoftusa.com

Windows is a registered trademark of Microsoft Corporation. Linux is a registered trademark of Linus Torvalds. All other names are trademarks of their respective owners.

Prices	Light	Standard	Professional
Layout		199\$	399\$
Layout + Schematic		398\$	798\$
Layout + Autorouter		398\$	798\$
Layout + Schematic + Autorouter	49\$	597\$	1197\$

Pay the difference for Upgrades

notation is a named association in which elements of an array are assigned by an index number or by the default name others.

You also could explicitly assign array elements with `0 => '0', 1 => '0', 2 => '0', and 3 => '0'`. A significant advantage of the others notation is that the array initializer can be independent of an array's size.

Vectors can be initialized using a constant bit vector such as `0000`. This approach reduces the amount of writing when initializing bit vectors. Extremely large bit vectors can be abbreviated even more by prefixing `x` for hexadecimal, `o` for octal, and `b` for binary so that `101010000001` can be written as `x"A81"` or `o"5201"`. The default bit vector radix is assumed to be base two.

The `clk`' event following the `elsif` makes use of a signal attribute. Refer to the *Circuit Cellar* FTP site for a list of some common VHDL attributes supported by most synthesis tools. The event attribute triggers the following statements whenever the attached

signal changes state. The `clk = '1'` condition means that the statements within the clock block, from then to end if, become active for every rising edge of the `CLOCK` signal. Synthesis tools look for this code sequence and produce clocked constructs in such cases. The `std_logic_1164` package defines two functions, `rising_edge` and `falling_edge`, which duplicate the rising edge statements' functionality. I'll address these functions with examples.

Basic counter functionality is defined by the central if, else, and end if statements. The if `enable = '1'` then clock enable statement provides a gated clock implementation to apply clock pulses to the counter only when the `ENABLE` pin is at a logical 1. Then, the counter state is incremented by one (an implicit conversion takes place to convert the one to a `std_logic_vector`) as long as the counter isn't equal to `1001` or nine, which represents the final decade counter state. When this final count is reached, the counter will perform a

synchronous reset on the next rising clock edge.

I know this may seem like a lot of work to get a decade counter, but it's all downhill from here. Armed with these basic concepts, you can design just about any counter or divider.

Figure 2 (page 44) shows the synthesized FPGA structure that results from this VHDL code. The primitives are based on those available in the Xilinx Spartan-3. As you can see, another benefit of VHDL is that you can express a design in a generic language that has no ties to a particular piece of hardware. You can resynthesize this same VHDL code for an Actel FPGA or any other vendor's device, including ASICs! Figure 3 (page 44) is a sample simulated output for approximately 10 clock cycles.

GENERIC ARGUMENTS

Generic arguments are powerful mechanisms available in VHDL for defining general-purpose entities that you can tailor to suit different requirements. For example, Listing 2 contains a generic counter implementation that's easily customized by passing a couple of arguments to transform it into practically every different counter or divider you'll need for my watch project!

Two generic arguments, `width` and `max_cnt`, which are located at the top of the entity declaration, are the keys to this flexibility. The former represents the counter's bit width. The default width is specified as eight. The `max_cnt` argument specifies the maximum count value that the counter can reach. The default `max_cnt` is 255. Default arguments enable you to create an instance without having to specify the generic arguments. As long as you're happy with the default generic arguments, neither the synthesis tool nor the simulator will complain.

The first place you'll see a change from the original decade counter is in the definition of the `q` signal. In the first decade counter implementation, I hard-coded an upper limit of three. Here in the port declaration, `q`'s upper limit is set to the value of `width-1`. Thus, if you were to instantiate this counter with a width of 12, `q`'s range would be 11 down to 0, thus creating a 12-bit counter width.

Listing 2—The general-purpose synchronous VHDL counter/divider implementation has generic parameters to specify the counter bit width and maximum count value. An asynchronous reset, a clock enable, and a carry output complete the design.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity divn is
    generic
        (width : integer := 8;
         max_cnt : integer := 255);
    port
        (clk : in std_logic;
         reset : in std_logic;
         enable : in std_logic;
         q : out std_logic_vector(width-1 downto 0);
         carry : out std_logic);
end divn;
architecture behav of divn is
    signal cnt : natural range 0 to max_cnt;
begin
    carry <= enable when cnt = max_cnt else '0';
    q <= conv_std_logic_vector(cnt, width);
    counter: process (clk, reset)
    begin
        if reset = '0' then
            cnt <= 0;
        elsif rising_edge(clk) then
            if enable = '1' then
                if cnt = max_cnt then
                    cnt <= 0;
                else
                    cnt <= cnt + 1;
                end if;
            end if;
        end if;
    end process;
end behav;
```

Another change relates to the data type used for the counter. The original decade counter used an `std_logic_vector` type. For the generic counter, however, I used a subtype of the natural number type for the `cnt` type. The subtype is declared implicitly in the `cnt` signal declaration as natural range 0 to `max_cnt`. This means that the `cnt` signal can take on any value from zero to `max_cnt`.

Why did I make this change? It certainly could have used an `std_logic_vector` as a generic argument, but I prefer working in base 10, so it made sense to use a natural number counter. There isn't a hardware

penalty for this choice. Plus it makes the design more readable. As a consequence, you need a conversion function (`conv_std_logic_vector`) to convert from the natural number `cnt` to the `std_logic_vector` result for `q`. The conversion takes place as part of the signal assignment where the `cnt` state is wired to the `q` output. The first argument is the natural or integer signal to be converted to a `std_logic_vector`. The second argument is the desired width of the resultant `std_logic_vector`. This conversion function is built into the IEEE `std_logic_arith` package.

The remaining code should look extremely similar to the decade counter (with the exception of using natural numbers in places where vector constants were previously required for initialization and maximum count comparison). Another change is the use of the `rising_edge` function to define the clock edge used for event transitions. This makes the code more easily understandable.

The final change has to do with the way you produce the carry output signal. In the decade counter, you simply use the most significant bit as the carry signal. But when creating a chain of synchronous counters, you might sometimes create counters in which the

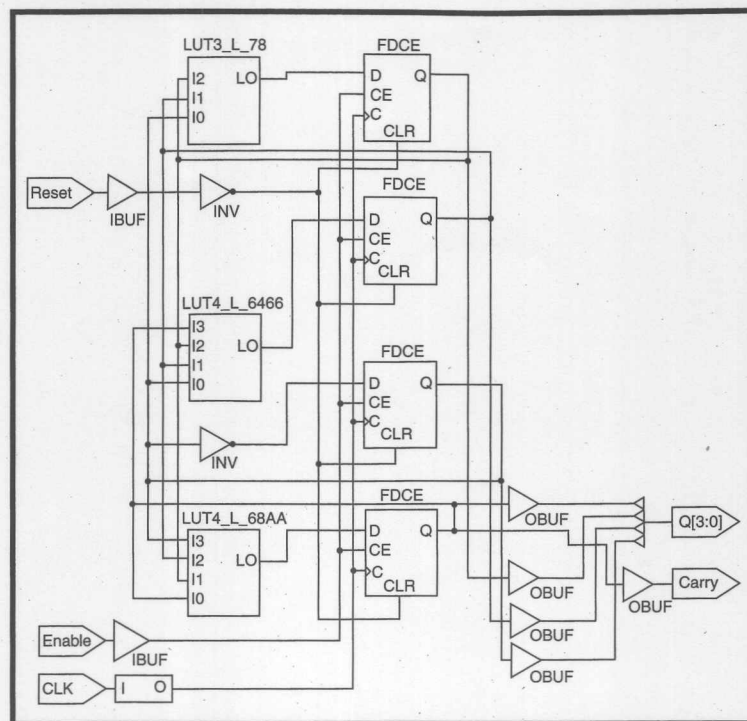


Figure 2—The Spartan-3 primitive blocks comprise the decade counter. The LUT3 and LUT4 blocks are three- and four-input look-up tables. The FDCE blocks are D flip-flops with clear and enable inputs.

upper bit remains high for longer than one clock cycle. Thus, you could get two or more clocks carrying through to the next counter in the chain.

Because you'll want only one carry clock generated each time the counter reaches its maximum value, that's what I encoded in the signal assignment for the carry output. Note that this is a conditional signal assignment using the `when` conditional statement. The `ENABLE` signal is passed through to the carry whenever the `cnt = max_cnt` condition is satisfied; otherwise, in the `else` clause, a logical 0 value is assigned to the carry.

FIRST TEST BENCH

You must create a test bench to test whether or not the generic counter

actually works. A test bench is analogous to a hardware bench. It contains instruments such as signal generators, oscilloscopes, and logic analyzers, which are connected to the circuit being tested. The VHDL equivalents of these instruments are shown in Listing 3.

A test bench is nothing more than an entity/architecture pair with the circuit being tested instantiated in the declarative region of the architecture. You can see the generic `divn` component declaration following the `is` of the architecture. Signal declarations for each of the `divn` port elements

follow the component. The actual instantiation is found in the architecture body beside the `uut :` label. Each signal passed or received from the `divn` port uses a named association with the port signal name on the left and the local signal on the right of the `=>` symbol.

The primary stimulus required is the clock, which is defined in the process block labeled "clock." Initially, `clk` is set to a logical 0 value.

The following `wait` statement pauses the process for 500 ns. The `wait` statement should never appear in any code that can be synthesized. After the first `wait`, `clk` is set to a logical 1 value and the process waits another 500 ns. After the final `wait` time has elapsed, the process begins executing from the

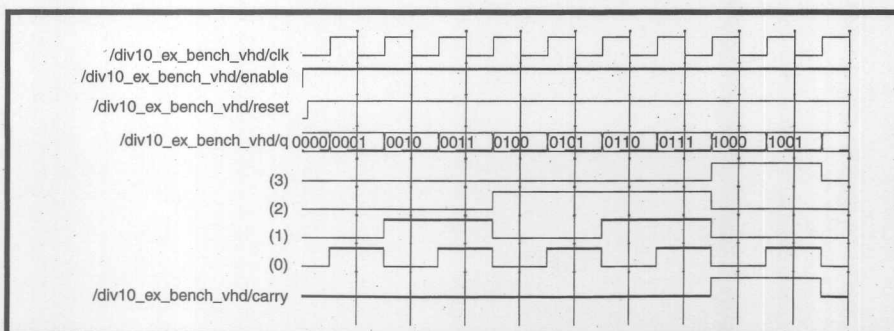


Figure 3—The top clock waveform drives the simulated decade counter. The `q` output is shown below in both a vector format and broken down into each of the four counter bits.

initial statement following the begin statement. In effect, this defined a clock with a 50% duty cycle and a 1- μ s period.

The second process, which is labeled tb, provides the required reset stimulus. Like clk, the reset receives an initial value of logical 0. After 100 ns, it's set to logical 1. The ENABLE signal is tied permanently to a logical 1 for the purposes of this test. The final wait statement with no arguments pauses the second process indefinitely. This is an effective method of execut-

ing the contents of a process only once. Remember, wait statements can't be synthesized and therefore can't appear in any VHDL intended to be rendered as a hardware component.

As you can see, by defining one or more processes and using wait statements, it should be possible to synthesize any stimulus required for driving a test component's inputs. More elaborate test benches can also include functional component models of elements such as memories, processors, clocks, and data acquisition systems provided by many

IC vendors. The simulator running the test bench acts as a logic analyzer and provides access to all the tested model's inputs and outputs.

START EXPERIMENTING

Thus far, I've covered a lot of VHDL territory: data types, attributes, entities, architectures, counters/dividers, generic components, test benches, instantiated components, and a variety of state-machines. Next month I'll investigate state machines, encoders/decoders, multiplexers, and ROMs. I'll show you how these elements can be combined to make the stopwatch application in Figure 1. Until then, download some VHDL tools and have fun experimenting with the examples in this article.

The complete VHDL source code is available on the *Circuit Cellar* FTP site. If you're using the Xilinx tool set, I also included a project that contains all the same source code. ■

Michael Griebeling is a professional electrical engineer with a B.A.Sc. in electrical engineering. He has been active in the aerospace industry for more than 20 years. Michael enjoys designing firmware, hardware, and software. You may reach him at mg@comp-inspirations.com.

PROJECT FILES

To download the code, go to ftp.circuitcellar.com/pub/Circuit_Cellar/2005/181.

RESOURCES

Std-1076-2002, *IEEE Standard Language Reference Manual*, IEEE, Piscataway, NJ, 2002.

Std-1164-1993, *IEEE Standard Multivalued Logic System for VHDL Model Interoperability*, IEEE, Piscataway, NJ, 1993.

Xilinx, *Spartan-3 FPGA Family: Complete Data Sheet*, DS099, January 2005.

——— *Spartan-3 Starter Kit Board User Guide*, UG130, Xilinx, October 2004.

SOURCES

ISE WebPACK 7.1i and XC3S200
Spartan-3 FPGA starter kit
Xilinx
www.xilinx.com

Listing 3—The small test bench generates CLOCK and RESET signals to drive the divn counter implementation. The test bench instantiates a decade counter from the divn generic counter.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.numeric_std.all;
entity divn_bench_vhd is
end divn_bench_vhd;
architecture behavior of divn_bench_vhd is
--Component declaration for the unit under test (UUT)
  component divn
    generic (width : integer;
             max_cnt : integer);
    port (clk : in std_logic;
          reset : in std_logic;
          enable : in std_logic;
          q : out std_logic_vector(width-1 downto 0);
          carry : out std_logic);
  end component;
--Inputs
  signal clk : std_logic := '0';
  signal reset : std_logic := '0';
  signal enable : std_logic := '0';
--Outputs
  signal q : std_logic_vector(3 downto 0);
  signal carry : std_logic;
begin
--Instantiate the unit under test (UUT)
  uut: divn
    generic map
      (width => 4,
       max_cnt => 9)
    port map
      (clk => clk,
       reset => reset,
       enable => enable,
       q => q,
       carry => carry);

  clock : process
  begin
    clk <= '0';
    wait for 500 ns;
    clk <= '1';
    wait for 500 ns;
  end process;
  tb : process
  begin
--Wait 100 ns for global reset to finish
    reset <= '0';
    enable <= '1';
    wait for 100 ns;
    reset <= '1';
    wait; -- will wait forever
  end process;
end;
```

Hardware Synthesis with VHDL (Part 2)

VHDL in Action

Ready to put VHDL in play? Michael shows you how to build state machines, decoders, multiplexers, debounce and edge detection circuits, tristate bus buffers, shift registers, and more.

Last month I described VHDL elements such as packages, entities, architectures, data types, attributes, and generic counters as an introduction to my watch application. Now I'll describe how you can build state machines, decoders, multiplexers, debounce and edge-detection circuits, tristate bus buffers, shift registers, and more.

WATCH BASICS

Let's begin by looking at the Watch component instantiation hierarchy (see Figure 1). The heart of the watch is the Time Base component, which takes a 50-MHz reference frequency from the Spartan-3 starter kit oscillator and divides it down to 1-kHz, 10-Hz, and 1-Hz reference enable clocks using a chain of dividers based on the Divn component. The 1-kHz ENABLE signal drives the display driver LED multiplexing. The 10-Hz ENABLE signal drives the stopwatch and debounce circuitry. The 1-Hz ENABLE signal provides a time base for both the normal date and time and the dual time zone functions, both of which are instantiated by the DateTime component.

The watch's brain resides in the Mode Generation component (see Listing 1, p. 50). The input push buttons and switches are debounced here. It's also where the Set Clock (PB1) push button's rising edge is detected. These inputs are decoded to provide the watch's different modes: the date/time function, the dual time zone, the stopwatch, and the alarm (see Table 1).

The Set Mode push button triggers the watch and alarm setting functions in Table 2. In Set mode, PB1 increments

the corresponding watch counter (seconds, minutes, hours, days, months, or years) by one each rising edge pulse.

BOUNCING SWITCHES

The debounce process in Listing 1 conditions the push button and switch inputs. Figure 2a shows a typical switch or push button waveform. Contact bounces occur on each make and break of the switch contacts. This bounce time can range from 5 to 50 ms, depending on the quality of the switch.

The 100-ms enable pulses are used to sample the switch and push buttons once every 0.1 s to filter out the contact bounce. The resultant output is a set of clean switch and push button pulses.

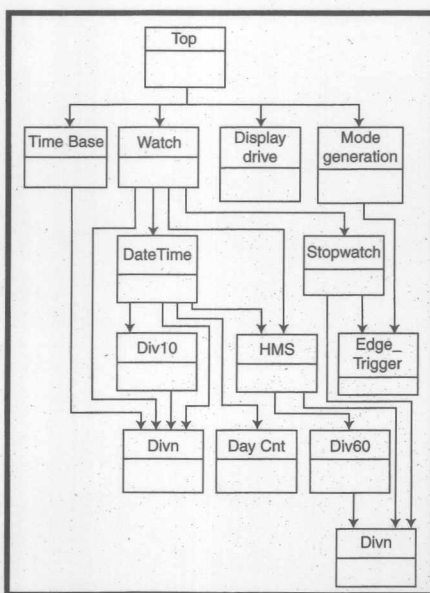


Figure 1—In the Watch component instantiation hierarchy, the Top component instantiates the Time Base, Watch, Mode Generation, and Display Driver components. The Divn and Edge_Trigger generic components are used throughout the watch application.

The en_debounce signal in Listing 1 occurs every 100 ms. The time base generates it. Both the pb_in and sw_in signal vectors are debounced and assigned to the pb and sw vectors, respectively.

DATE/TIME SELECTION

Unfortunately, the Spartan-3 starter kit provides only a four-digit LED display. Thus, to display both the time and date (as most watches do), you need a way to select which output is displayed on the LED.

The ToggleDateTime process in Listing 1 accomplishes this by toggling between modes that display either the time or date. PB3 switches between displaying the time or date for both the normal date/time and the dual date/time functions with each activation.

The ToggleDateTime process is different from most others because it involves a second clock source (i.e., PB3) to drive the dtime signal toggling. Furthermore, this push button is active only for this function while either of the two date/time modes are displayed. Note that only the watch modes change within the Mode Generation component. We'll look at the actual display multiplexing in the Display Driver component.

ON THE EDGE

There are two methods for triggering on a particular edge of an input: either clock a process directly (as I demonstrated with the Date/Time select) or use an edge-detection circuit (see Listing 2, p. 52). An example of how the edge detection works is shown in Figure 2b. The asynchronous input sig-

nal is first clocked to generate a clock-synchronous signal. The synchronous signal is then delayed by one clock cycle.

To decode a rising edge signal, use the equation $x_edge \leq x_syncd$ and not $x_delayed$. A falling edge is decoded with the equation $x_edge \leq \text{not } x_syncd$ and $x_delayed$.

Like the Divn component, the Edge_Trigger component has a generic input called `rising_edge_pulse`. This component will detect a rising edge if a logical 1 is passed to this port; otherwise, it detects a falling edge.

COMPONENTS

The Watch component interconnects the DateTime, HMS, and Stopwatch components. The HMS instance implements the alarm.

Two instances of the DateTime component become the current date and time and the dual time zone. The HMS instance is used as the central alarm.

The snooze function is implemented in the Watch component. The actual alarm function is contained in the individual DateTime components. The alarm signal is sent back to the Watch component. There are two possible alarm sources from either the current date/time or the dual time zone, so these signals are combined at the Watch level. After the alarm is activated, you have the option of activating a snooze counter (derived from the Divn component) with a 10-min. time out period. A state machine implements the alarm and snooze functions. The alarm reactivates after the snooze counter times out. The alarm can be cleared with SW3 or the snooze counter can be restarted with PB2 for another 10-min. period.

The DateTime component instantiates Divn- and Div10-based compo-

Function	SW0	SW1	SW3	SW4	PB0	PB1	PB2	PB3
Date/time	0	0	Alarm on/off	12/24 Hours	Toggle Set mode	Set increment	Snooze	Toggle date/time
Second time zone	1	0	Alarm on/off	12/24 Hours	Toggle Set mode	Set increment	Snooze	Toggle date/time
Alarm display	0	1	Alarm on/off	12/24 Hours	Toggle Set mode	Set increment	—	—
Stopwatch	1	1	—	—	Reset	Start/stop	Lap	—

Table 1—The watch application's modes determine which of four functions are displayed on the four-digit output LED and control the component used during the watch-setting operation.

nents that implement the majority of the date and time counters. This component is also responsible for checking when the alarm matches the current hours and minutes via the CheckAlarm process posted on the *Circuit Cellar* FTP site. During synthesis, the = operator produces hardware that compares the alarm signal to the active hour/minute signal. When the two signals are equivalent, the `alarm_on` signal is activated.

The date is probably the trickiest part of the DateTime function. You must automatically adjust the number of days in a month, calculate whether or not the current year is a leap year, and remap both the month and day counters to start from a count of one instead of zero.

The month remapping listing is posted on the *Circuit Cellar* FTP site. A counter range from zero to 11 is mapped to a binary-coded decimal month number that ranges from x01 to x12.

I couldn't use the Divn component for the day counter. Because the maximum day count changes from month to month, the day maximum value must be variable. The `day_cnt` component implements this function. In addition to the normal arguments of the Divn counter instances, I provided a maximum count value input.

I needed to be innovative with the year counter. First, I used two Div10 (decade) counters to implement the units and tens places in the year. Then the "20" century was hard-coded to expedite the year-setting process. Instead of having to start from a year of zero and increment 2,000 times to reach the right century, you start at a count of 2,000 and increment to the current year. Only years from 2000 to 2099 can be supported. Leap year cal-

culations require a second, 2-bit binary year counter that effectively performs a modulo four operation on the year. The reason this works is that the year 2000 mod 4 equals zero, so both the BCD counters and the binary counter can start from zero. They're guaranteed to synchronize as the year is set.

I haven't implemented a day of the week function mainly because there isn't a nice way to display the result with the Spartan-3 starter kit. Most watches cheat and require you to set the current day of the week along with the date. I would prefer to have this value calculated automatically from the current date. I'll leave this implementation for you to work out.

Also, it would be useful to add a feature that automatically adjusts for daylight saving time. This function would require the correct day of the week, so I omitted it in this watch implementation. Again, it's fairly simple to add, so I'll leave it for you to implement.

The LED display has only four digits. So, how do you display the hours, minutes, and seconds? The solution I came

Function	mode(6)	mode(5)	mode(4)
Normal timekeeping	0	0	0
Set seconds	0	0	1
Set minutes	0	1	0
Set hours	0	1	1
Set days	1	0	0
Set months	1	0	1
Set years	1	1	0

Table 2—Seven watch-setting modes give you the ability to preset the seconds, minutes, hours, days, months, and years of the currently selected function. The active Set mode is displayed using discrete output LEDs (LED7, LED6, and LED5.)

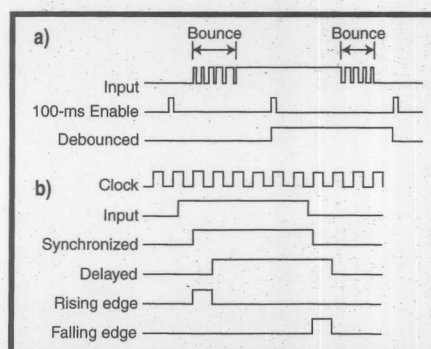


Figure 2a—The topmost input signal exhibits bounce during switch make and break transitions. By sampling the input signal at 100-ms intervals, a debounced signal is generated. **b**—These timing waveforms show how the edge detection is accomplished. By properly decoding a delayed and clock-synchronous signal, you can generate either a rising- or falling-edge pulse.


ACONTM

DC-DC CONVERTERS

DC-DC CONVERTER

Single Output

 - ▶ 1.2V
- ▶ 1.5V
- ▶ 5.0V
- ▶ 7.5V - 10V



25 watt, 5 Output

- ▶ 24V
- ▶ 28V
- ▶ 48V
- ▶ 60V - 80V

Dual Output

Triple Output

Quad Output

Five Output

300 Vdc Input

PoE (Power over Ethernet)

Chassis Mountable

ACON Converter Series

Request for Custom Design

Technical Documentation

© ACON, INC., 2005

Over 2,000 Models

- Open Frame & Encapsulated
- Input Range : 9 to 420 Vdc
- Output Voltage : 1.2 to 80 Vdc
- Number of Output : 1 to 5
- Output Power : 2 to 300 Watts

ACON inc

South Easton, MA 02375

Toll Free: 1-800.336.8022

Web: www.aconinc.com

E-Mail: Sales@aconinc.com

up with was to automatically switch between an hours/minutes display and a minutes/seconds display every 5 s. As well, the date display needs to switch between displaying the day/month and

the year. A secondary function, when setting the date/time, requires that the correct quantity (seconds, hours, etc.) be displayed. The DriveDisplay process in the DateTime component imple-

Listing 1—The mode generation component conditions the input push buttons and switches. It also generates the watch modes to control the watch functions.

```
architecture behav of mode_generation is
--Declarations omitted for clarity
begin
--Generate single rising-edge pulse for set push button
gen_set_pb: edge_trigger
port map (
clk => clk,
reset => reset,
x => pb(1),
x_edge => mode(7)
);
--Inputs are debounced by sampling inputs every 100 ms, thus
--ignoring bounce transitions within this period.
debounce: process (reset, clk)
begin
if reset = '0' then
pb <= (others => '0');
sw <= (others => '0');
elsif rising_edge(clk) then
if en_debounce = '1' then
pb <= pb_in;
sw <= sw_in;
end if;
end if;
end process;
--Generate the mode signals
--Omitted for clarity
GenSetMode: process (set_clk, reset, min_sel)
begin
if reset = '0' then
setmode <= min_sel;
elsif rising_edge(set_clk) then
if setmode = max_sel then
setmode <= min_sel;
else
setmode <= setmode + 1;
end if;
end if;
end process;
GenMinMax: process (sw)
begin
case sw(1 downto 0) is
when "00" | "01" =>
min_sel <= "000"; --Clock and dual-time can set seconds to years
max_sel <= "110";
when "10" =>
min_sel <= "000"; --Alarm can set seconds to hours
max_sel <= "011";
when others =>
min_sel <= "000"; --Stopwatch can't be set
max_sel <= "000";
end case;
end process;
ToggleDateTime: process (set_dt, reset)
begin
if reset = '0' then
dtm <= '0';
elsif rising_edge(set_dt) then
if tm_en = '1' then
dtm <= not dtm;
end if;
end if;
end process;
end behav;
```


M16C

PLATFORM

Everywhere you imagine. **RENESAS**

*MCU Solutions Matched
To Your Design Imagination*

RENESAS IS THE #1 MCU SUPPLIER IN THE WORLD. www.renesas.com

M16C Advantages

- Advanced 16-bit and 32-bit CISC cores that perform at up to 32 Dhrystone 1.1 MIPS
- Banked-register architecture optimized for fast context switching
- Wide range of high-performance flash memory: 8 KB to 512 KB
- Best-in-class EMI/EMS noise immunity
- Designed to be pin- and function-compatible between families and packages
- Extensive peripheral integration: everything from POR and LVD to CRC counters

Low-cost Renesas Toolchain

- Fully integrated suite of hardware and software tools
- Highly-optimized C compiler and assembler — FREE (64K limited version): Download latest version from web (www.renesas.com/skp)
- Low-cost Starter Kit (target board, USB debugger, complete toolchain), starting at \$49
- Easy online access to application notes, example code, software development tools

*Get your product to market faster
using Renesas Interactive!*



*Evaluate, test, and learn
about Renesas products
in an interactive online
environment.*

www.renesasinteractive.com

SKP	Device	C Compiler, Assembler, IDE	Cost
SKP8CMINI13	R5F21134FP	FREE (64K limited version)	\$49
SKP8CMINI17	R5F21174FP		\$49
SKP16C26A	M30260F8AGP		\$49
SKP16C28	M30280FAHP		\$49
SKP16C62P	M30626FHPFP		\$49
SKP32C83	M30835FJGP		\$119
SKP32C84	M30845FJGP		\$49

Special pricing is in US dollars from Renesas authorized North American distributors only, and is subject to change.

Popular Devices

Series/ Group	Part Number	CPU (Bits)	Package	Freq. (MHz)	Dhrystone 1.1 MIPS (Max)	Program Flash (KB)	Data Flash (KB) (10K Rewrites)	SRAM (Bytes)	Serial I/O Channels	I ² C	I/O	A/D 10-bit	Ring Osc.	LVD POR	Timers	Price *
R8C/17	R5F21172SP	16	20 Pin SSOP	20	9	8	2	512	1	1	15	4	X	X	3+WDT	\$1.90*
R8C/13	R5F21134FP	16	32 Pin LQFP	20	9	16	4	1K	2	—	24	12	X	X	4+WDT	\$2.38*
M16C/26A	M30260F8AGP	16	48 Pin LQFP	20	13	64	4	2K	3	1	39	12	X	X	8+WDT	\$4.76*
M16C/28	M30281FAHP	16	64 Pin LQFP	20	13	96	4	8K	4	1	55	13	X	X	9+WDT	\$5.90*
M16C/62P	M30624FGPGP	16	100 Pin QFP	24	16	256	4	20K	5	3	87	26	X	X	11+WDT	\$8.25*
M16C/62P	M30626FHPGP	16	100 Pin QFP	24	16	384	4	31K	5	3	87	26	X	X	11+WDT	\$10.05*
M32C/84	M30845FJGP	16	144 Pin LQFP	32	32	512	—	24K	5	5	124	34	X	X	11+WDT	\$16.88*

* Suggested 10,000 piece price. Please contact your local Renesas distributor for volume pricing.

Listing 2—Take a look at the VHDL implementation of an edge-detection function. The first process samples the input signal on the clock's rising edge to provide a clock synchronous signal (*x_synced*). The *x_synced* signal is then delayed by one clock cycle and assigned to the *x_delayed* signal. In the second process, either a rising or falling edge pulse (*x_edge*) is generated depending on the *rising_edge_pulse* generic parameter.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity edge_trigger is
  generic (rising_edge_pulse : std_logic := '1');
  port (clk : in std_logic;
        reset : in std_logic;
        x : in std_logic;
        x_edge : out std_logic);
end edge_trigger;
architecture Behavioral of edge_trigger is
  signal x_synced : std_logic;
  signal x_delayed : std_logic;
begin
  process (clk, reset)
  begin
    if reset = '0' then
      x_synced <= '0';
      x_delayed <= '0';
    elsif rising_edge(clk) then
      x_synced <= x;
      x_delayed <= x_synced;
    end if;
  end process;
  process (x_synced, x_delayed)
  begin
    if rising_edge_pulse = '1' then
      x_edge <= x_synced and not x_delayed;
    else
      x_edge <= not x_synced and x_delayed;
    end if;
  end process;
end Behavioral;
```

ments this display switching.

Another complication relates to the 12- and 24-h support implemented in the Hour/Minute/Second (HMS) component. The actual hour counter has a range from zero to 23. In 12-h mode, this range is mapped to binary-coded decimal values from x01 to x12 in two ranges, with the second range marked with a p.m. indicator. In 24-h mode, you end up with binary-coded decimal values from x00 to x23. In effect, the encoder implements a binary-to-binary-coded decimal decoder. The full code is posted on the *Circuit Cellar* FTP site.

STOP TIME

Let's look at the stopwatch in Listing 3 (p. 54) in some detail. It contains a state machine implementation and instantiates an Edge_Trigger component. At the top of the architecture declaration are both the Divn and Edge_Trigger components. Following these components is the first enumerated type declaration called the *sw_state_type*. It consists of three enumerated names (*sw_idle*, *sw_running*, and *sw_freeze*), one

Large Data Has Met Its Match

**RCM3365 RabbitCore With 'Hot-Swappable'
Removable Memory**

Designed to meet the demanding needs of data-intensive applications, the RCM3365 delivers great flexibility with on-board NAND Flash and a memory card socket.

RCM3365 Features

- Rabbit 3000 @ 44.2 MHz clock
- 52 digital I/O
- 10/100Base-T Ethernet
- 512K SRAM and 512K Flash
- 16 MB NAND Flash
- "Hot-swappable" memory card socket (supports 128 MB memory card)

Free Design Book!

Get started with the RCM3365 RabbitCore development kit that includes hardware and software tools.

www.3365rcm.com



2932 Spafford Street
Davis, CA 95616
530.757.8400

9965

It gets no easier than this!


SPLat is an innovative new set of solutions that's changing how OEMs world-wide think about embedded controls. With SPLat you can program a quick and dirty sequencer literally in minutes, yet the power is there to make sophisticated state machine based multi-tasking systems with elegant user menus and floating point arithmetic. Our hardware comes with real-world I/O interfaces, ready to wire in, straight out of the box. We have a wide range of special function add-ons for hard to implement tasks like AC current measurement and DC motor control. Best of all, you can do a proof of concept using off-the-shelf product and later migrate all your knowledge and 98% of your code to a fully customized SPLat controller for quantities down to a few hundred. Check out our website today!

Example: SPLat MS120EM216

- 12 digital I/Os *plus*
- 2x16 LCD, blue backlight
- 5 push buttons
- 4 programmable LEDs
- Expandable



Ph. (781) 729-3005

 

\$99
Qty 1

www.splat-cc.com

for each of the states of the stopwatch state machine in Figure 3. The state and next_state signal declarations are defined with the sw_state_type. They hold the current and next states for the stopwatch.

Within the body of the architecture, the Edge_Trigger component is instantiated twice, once for each of the push buttons that control the stopwatch. You need to detect the rising edge transition for these signals because you don't want the state machine to oscillate between states while a push button is held in the on state. Unless an edge is used, this is a distinct possibility because the same signal is used as a transition gate to both exit and enter the same state.

The state machine consists of three processes: sync_proc, output_decode, and next_state_decode. The sync_proc process updates the state machine's current state on each rising edge of the clock. The output_decode process generates the stopwatch outputs, which consist of the count_enable signal to enable the clocking of the stopwatch counters at a 10-Hz rate. The external display signal is updated whenever the stopwatch is running or in the idle state. The lap function is implemented by having the stopwatch counters continue to run while in the freeze state even though the actual display remains latched with the previous active stopwatch count. The next_state_decode process determines the value of the next_state signal based on the current state and the start_edge/pause_edge signals. A case statement mirrors the state machine states and if/elsif statements select the values for the next_state signal.

When synthesized, simple state machines are usually implemented as a "one-hot" counter chain. This means that there is one state per register. For state machines with a few states, this is usually an optimal approach because no state decoding is required. State outputs can be generated directly from each of the state registers. Most synthesis tools also give manual control of the state encoding mechanism. Typical options are Gray code, Compact, Sequential, Johnson, One-Hot, and User-defined state encodings. Refer

to your favorite tool's documentation for details on how to set these options.

DRIVE THE DISPLAY

The final component in the watch application is the Display Driver component. It decodes the binary-coded decimal display signal into a

seven-segment display signal that physically drives the multiplexed LED. Multiplexing drives a single digit of the display at a time so that wiring is minimized. By rapidly sequencing the four digits (at 1 kHz in this case) with the correct information, due to the eye's persistence of vision, the display gives

Listing 3—*The complete VHDL stopwatch implementation contains divn and edge_trigger instances. An internal state machine implementation controls how the counters are incremented and displayed on the four-digit external display. User interaction with the state machine gives the stopwatch's functionality.*

```
architecture behav of stopwatch is
    component divn
    --Code removed: See full listing on the Circuit Cellar FTP site
    end component;
    component edge_trigger
    generic (rising_edge_pulse : std_logic := '1');
    port (clk, reset, x : in std_logic; x_edge : out std_logic);
    end component;
    --Stop watch state definitions
    type sw_state_type is (sw_idle, sw_running, sw_freeze);
    signal state, next_state : sw_state_type;
    --Code removed: See full listing on the Circuit Cellar FTP site
begin
    --Generate rising edge pulses for inputs
    gen_start: edge_trigger
    port map (clk => clk, reset => reset,
        x => start_stop, x_edge => start_edge);
    gen_pause: edge_trigger
    port map (clk => clk, reset => reset,
        x => pause, x_edge => pause_edge);
    --Code removed: See full listing on the Circuit Cellar FTP site
    --Stop watch state machine
    SYNC_PROC: process (clk, reset)
    begin
        if reset = '0' then
            state <= sw_idle;
        elsif rising_edge(clk) then
            state <= next_state;
        end if;
    end process;
    --MEALY state machine. Outputs are based on state and inputs
    OUTPUT_DECODE: process (state, enable, stop_watch)
    begin
        if state = sw_idle then count_enable <= '0';
        else count_enable <= enable;
        end if;
        if state = sw_running or state = sw_idle then
            display <= stop_watch;
        end if;
    end process;
    NEXT_STATE_DECODE: process (state, start_edge, pause_edge)
    begin
        next_state <= state; --default is to stay in current state
        case state is
            when sw_idle =>
                if start_edge = '1' then next_state <= sw_running;
                end if;
            when sw_running =>
                if start_edge = '1' then next_state <= sw_idle;
                elsif pause_edge = '1' then next_state <= sw_freeze;
                end if;
            when sw_freeze =>
                if start_edge = '1' then next_state <= sw_idle;
                elsif pause_edge = '1' then next_state <= sw_running;
                end if;
        end case;
    end process;
end behav;
```

the appearance of having all four digits on at the same time. A four-digit multiplexed LED requires only 12 connections: four digit drives and eight segment drives (one drives the decimal point). Without multiplexing, the same four-digit LED would require 32 separate connections.

To aid in setting the internal date/time, a flashing function turns on and off pairs of digits in response to the watch's mode. When an alarm is active, all the digits flash. The flashing operation uses a specially encoded segment drive value corresponding to an "1111" input that turns off all the segments. A 1-Hz signal controls the display flashing rate. Refer the *Circuit Cellar* FTP site for the complete VHDL source code for the Display Driver component.

TRISTATE BUFFERS

Although not used in the watch application, it's fairly common to have an FPGA connect to a data bus that's shared with multiple components such as memories, microprocessors, or data acquisition systems. So, how do

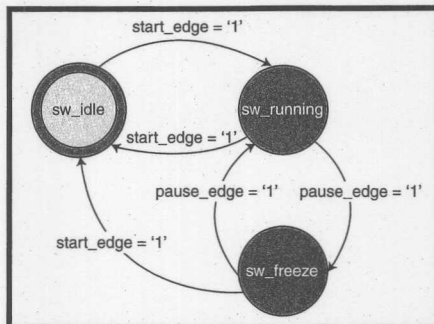


Figure 3—In the stopwatch state machine, two control inputs (*start_edge* and *pause_edge*) cause transitions among the *sw_idle*, *sw_running*, and *sw_freeze* states.

you implement this with VHDL?

The 8-bit tristate buffer posted on the *Circuit Cellar* FTP site reads from and writes to a shared data bus. A READ signal latches the bus contents into an internal register. This is also a typical VHDL latch implementation. A WRITE signal enables the tristate buffer and places the input register's contents on the bus as long as the WRITE signal is active.

Tristate buffers can be implemented only on the external I/O pins of an FPGA. The synthesis tools will auto-

matically "bubble up" tristate pins to the top level of a design so that they are located on external connections.


SHIFT REGISTERS

Implementing a shift register in VHDL is fairly straightforward: Define a vector whose size reflects the number of bits in the desired shift register and use a clocked process to shift the register contents 1 bit at a time. To shift a single bit left, write: `reg <= reg(14 downto 0) & '0'`. Here, the uppermost bit, or `reg(15)` (assuming a 16-bit shift register), is shifted out of the register and a logical 0 is shifted into the least significant bit position.

To reverse the direction of the shift register, write: `reg <= '0' & reg(15 downto 1)`. Some vendors have specific FPGA constructs that efficiently implement shift registers. For example, the Spartan-3 uses an SRL16 component to implement efficient shift registers with up to 16 bits. A popular use of shift registers is to serialize parallel data streams and convert serial communication streams into parallel data.

Fanless Super-computing!

 Combining the very best of high performance Intel® Pentium® M technology and the industry standard EBX format...



APOLLO

- Intel® Pentium® M or Intel® Celeron® M processors
- 600MHz to 2.1GHz
- Up to 1024Mbytes DDR memory
- Intel Extreme Graphics 2 dual video outputs (CRT & LVDS)
- Dual Ethernet - 10/100baseTx standard (option for 1000baseT)
- Six USB 2.0 channels
- Two IEEE1394a-2000 Firewire Ports (100/200/400Mbps)
- Ideal for high performance compact systems with restricted ventilation
- PCibus and CompactFlash (CF+) expansion
- Also available: 1U 19" rackmount enclosure



www.arcom.com

Development Kits ☒ Embedded Boards ☒ PCs & Enclosures ☒ Industrial Networking ☒ Design & Build ☒

Arcom

us-sales@arcom.com
888-941-2224

Think Embedded.
Think Arcom.

RAM & ROM

Many FPGAs include memory elements as part of their design. With a proper design, memories can be inferred from the VHDL code by the synthesis engine. For example, to implement an 8 x 8 bit ROM element, start with a type declaration such as `Mem_type = array (0 to 7) of std_logic_vector(7 downto 0)`. Next, a constant with the `Mem_type` needs to be declared along with an initialization constant array: `constant rom : Mem_type := (x"10", x"20", x"30", x"40", x"50", x"60", x"70", x"80")`. For example, the fourth byte of the rom constant is accessed as `rom(3)`.

Implementing a RAM is similar, except a signal declaration is used instead of a constant: `signal ram : Mem_type`. No initialization constant array can be used with RAM. Accesses to the RAM can be either synchronous to a clock or asynchronous, depending on the application. The synchronous RAM needs to be contained within a clocked process while the asynchronous RAM can appear in any statement.

MATH FUNCTIONS

Vendors such as Xilinx include hardware multipliers within their FPGA fabric. For example, the XC3S200 FPGA included with the evaluation kit contains 12 18 x 18 bit signed multipliers, each of which produces a 36-bit result. Implementing math functions is fairly easy: just use whichever operator (+, -, *, mod, or /) you require as part of a statement and the synthesis tool will automatically instantiate the appropriate integer math hardware. Of course, indiscriminate use of math operators is guaranteed to quickly chew up FPGA resources, so you may need to make some trade-offs such as sharing math hardware through the use of multiplexers.

BRIDGING CLOCK DOMAINS


In the real world, it is necessary to deal with events that occur on different time scales. For example, in the stopwatch, it was necessary to interface a 10-Hz counter chain with push button controls operated asynchronously by a human. Whenever two or more different clock domains interact,

some sort of bridging mechanism is required to ensure that timing glitches can't occur. Recall the edge detection circuit I used to condition the push buttons. The inputs were first synchronized to the clock, and then they were delayed or latched. Latches are a common mechanism to transition between clock domains. Other bridging mechanisms include FIFOs and dual-ported memories.

With a FIFO, data is written in with a first clock, and data is read out with a second clock. Obviously, some synchronization is also required to ensure that the FIFO doesn't overflow and that the reader doesn't run out of data.

A dual-ported memory gives simultaneous access to a shared memory array. Two separately clocked processes can independently access the memory in either Read or Write modes. Of course, some discipline is still required to prevent one process from overwriting data placed in the memory by the second process. Typically, different memory regions are read-only for process one, can be read or write for

HomeVision-Pro

 

CONTROLS:


- ◆ Lighting
- ◆ HVAC
- ◆ Security
- ◆ A/V
- ◆ Much more...

HomeVision-Pro is the newest, most powerful automation controller in the award-winning HomeVision® product line. It's configured from a PC, but can then run standalone. Features:

- ◆ Two-way X-10 & IR
- ◆ Video screens on a TV
- ◆ 8 relays
- ◆ 16 digital & 4 analog I/O
- ◆ 64 digital temp sensors
- ◆ 1 USB & 3 serial ports
- ◆ Powerful scheduling (>8000 lines, >2000 objects)
- ◆ Clock
- ◆ PC web server
- ◆ Expandable
- ◆ Software included
- ◆ 3-year warranty

Custom Solutions, Inc.

 800-398-8882, Web: www.csi3.com, E-mail: csi@csi3.com



KEYNOTE SPEAKER



Dr. Andrew J. Viterbi
Pioneer in Wireless Communications,
co-founder of QUALCOMM and
creator of the Viterbi Algorithm

GSPx 2005 is the only independent conference and expo where the signal processing community sees the latest ideas, innovations and products in a single event.

GSPx 2005

Pervasive Signal Processing

Oct. 24 - 27, 2005 • Santa Clara, CA USA

GSPx 2005 conference and expo focus on the following vertical areas:

• Video Compression

VC-1 Dr. Sridhar Srinivasan, Microsoft Corporation
H.264 / MPEG-4 AVC Coder Dr. Marta Karczewicz,
Senior Research Manager at Nokia Research Center

• Wireless

Wimax Mr. Naftali Chayat, Chief Scientist at Alvarion
UWB Mr. Patrick Kinney, Chair IEEE 802.15 TG4a

• S.A.R. Imagery

Dr. Chris Oliver, CBE, Leader in SAR Imaging

• Multicore

Dr. Winthrop W. Smith, Chief Engineer / Scientist
Raytheon Company

Technical Workshop by: Annapolis Micro Systems, BDTI, Celoxica, Intel, MathWorks, Synplicity

Register Now at www.gspix.com to attend the expo and to get key insights from experts through tutorials, workshops and panels.

To become a Sponsor email sales@gspix.com

GSPx 2005 is sponsored by the following companies:



process two to prevent write conflicts.

FPGA vendors have FIFO and dual-ported memory solutions specific to their FPGAs. These implementations may make use of special memory arrays in the FPGA fabric, or they may use distributed register-based memory implementations. You'll need to consult your FPGA's documentation to know how to best implement these functions.

VHDL WRAP-UP

In case you're interested, the final watch project used the following resources in an XC3S200-4FT256C FPGA: slice registers (4% used out of 3,840), four-input LUTs (15% used out of 3,840), I/O (19% used out of 173), and global clocks (12% used out of 8). This is the second smallest FPGA in the Spartan-3 family, so you can imagine the amount of functionality that could fit in some of the larger family members with more than 10 times these resources. The maximum estimated speed of this design clocked in at about 76.5 MHz.

Although I've covered a lot of the VHDL language, a great deal remains

unsaid. I haven't covered clock synthesis, constraints, and I/O interfacing. The main reason for this is that these topics are extremely dependent on a particular vendor's FPGA implementation. I have also deliberately skimmed over the topics that are required to produce functional VHDL models for simulation. My goal has been to introduce enough VHDL background to provide a solid foundation for hardware synthesis so that a more detailed exploration of VHDL with a particular vendor's toolset is possible.

The cost of using custom FPGAs has been steadily decreasing to a point where it is now possible for hobbyists to include these devices in their designs. VHDL provides a powerful high-level and machine-independent tool to define hardware within these FPGAs. I hope you've found this introduction to VHDL informative and will continue exploring this fascinating subject. ■

Michael Griebeling is a professional electrical engineer with a B.A.Sc. in electrical engineering. He has been active in the aerospace industry for more than 20

years. He enjoys designing firmware, hardware, and software. You may reach him at mg@comp-inspirations.com.

PROJECT FILES

To download the code, go to ftp://ftp.circuitcellar.com/pub/Circuit_Cellar/2005/182.

RESOURCES

Std-1076-2002, *IEEE Standard Language Reference Manual*, IEEE, 2002.

Std-1164-1993, *IEEE Standard Multivalued Logic System for VHDL Model Interoperability*, IEEE, 1993.

Xilinx, *Spartan-3 FPGA Family: Complete Data Sheet*, DS099, Jan. 2005.

——, *Spartan-3 Starter Kit Board User Guide*, UG130, Xilinx, Oct. 2004.


SOURCE

ISE WebPACK 7.1i and XC3S200
Spartan-3 FPGA starter kit
Xilinx
www.xilinx.com



DYNON INSTRUMENTS

A Complete Electronics Lab for \$495

 

ELAB-080

Includes 5 Instruments

- 2 Channel 80 MHz Digital Storage Oscilloscope
- 16 Channel Logic Analyzer, Synchronous with DSO
- Arbitrary Waveform Generator
- 2 Programmable Power Supplies
- 2 Programmable Clocks

Plus....

- Powerful PC User Interface Program
- Probes
- Cables

Now includes FFT!

www.dynoninstruments.com

Woodinville, WA 98072 (425) 402-0433